

Student ID:		
Family Name:		
Other Name:		
Desk:	n/a	
Date:		
Exam Mark:		

In-Workshop Examination, WRKXX, Week W, Semester 2, 20YY

Computer Systems COMP SCI 2000, 7081

Official Reading Time: none
Writing Time: 40 mins
Total Duration: 40 mins

Questions	Time	Marks
Answer all 6 questions	40 mins	40 marks 40 Total

Instructions for Candidates

- This is a closed book exam.
- Answer all questions in the spaces provided.
- Examination material must not be removed from the examination room.
- You must attend your enrolled workshop.
- A student ID card must be displayed at all times.
- No calculators or other electronics are permitted.
- Mobile phones must be turned off.
- Personal effects may be kept in a bag but, this must be placed on the floor.
- No talking or looking at other student's work.

Permitted Materials

- Foreign language paper dictionaries permitted.

DO NOT COMMENCE WRITING UNTIL INSTRUCTED TO DO SO

Question 1

Using only Nand gates, draw the logic circuit and write HDL code for the And gate. Clearly label the internal wires with the names used in your HDL.


HDL

```
Chip And
{
    IN a, b ;
    OUT out ;
} // The available chips:
      // Nand(a=? ,b=? ,out=?)
```

PARTS:

// write your HDL code in this box

}

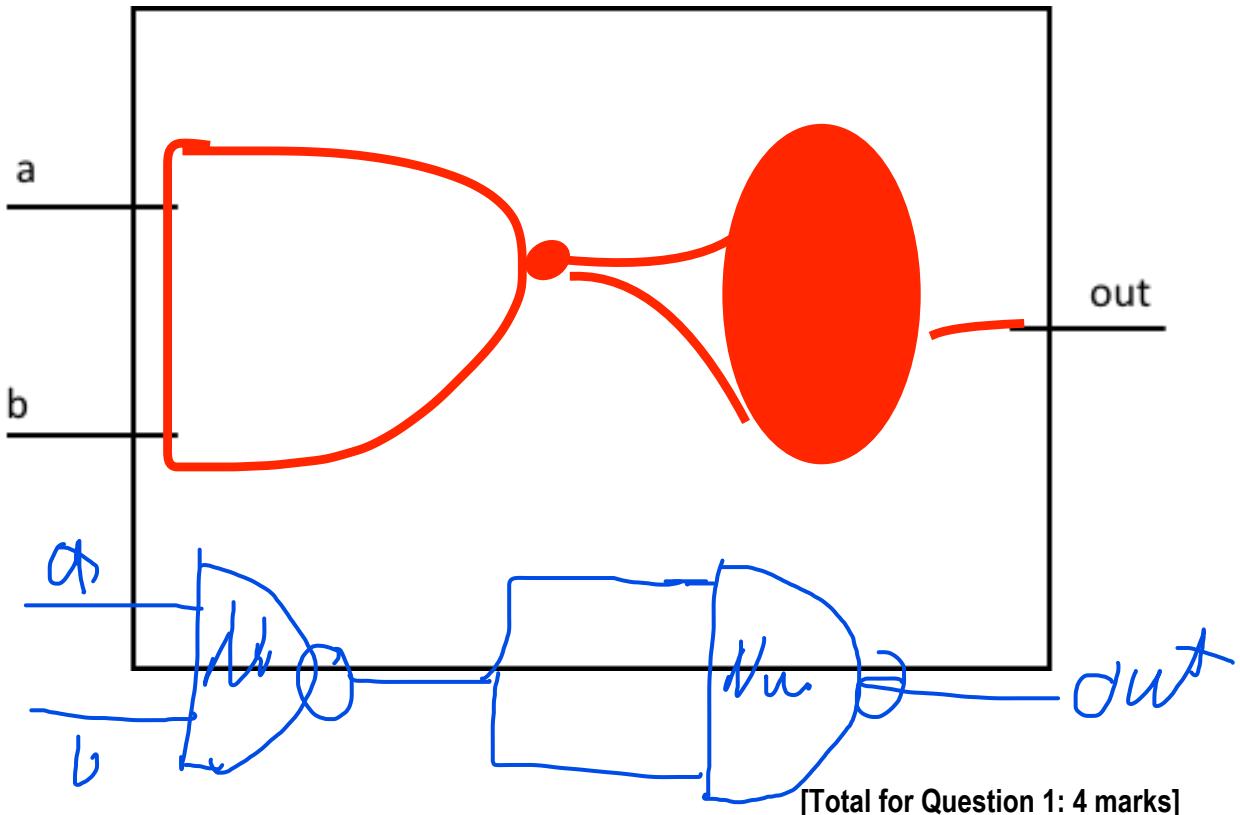Circuit Diagram**Available chips:**

Question 2

Using only Nand gates, draw the logic circuit and write HDL code for the Or gate. Clearly label the internal wires with the names used in your HDL.


HDL

```
Chip Or          // The available chips:  
{                // Nand(a=? ,b=? ,out=? )  
    IN a, b ;  
    OUT out ;
```

PARTS:

// write your HDL code in this box

}

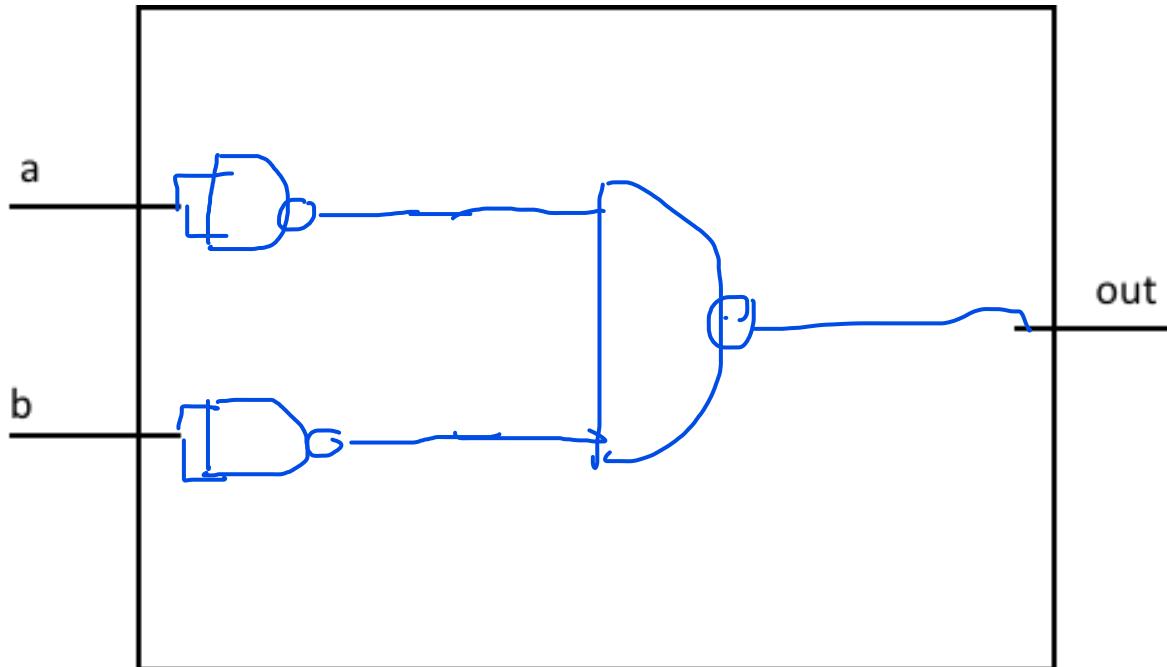Circuit Diagram**Available chips:**

[Total for Question 2: 6 marks]

Question 3

Using only And, Or and Not gates, draw the logic circuit and write HDL code for the Xor gate. The Xor gate for two values a and b must be implemented as: $a \cdot \bar{b} + \bar{a} \cdot b$. Clearly label the internal wires with the names used in your HDL.



HDL

```
Chip Xor                                // The available chips:  
{                                         // And(a=? ,b=? ,out=? )  
    IN a, b ;                           // Or(a=? ,b=? ,out=? )  
    OUT out ;                          // Not(in=? ,out=? )
```

PARTS:

// write your HDL code in this box

}

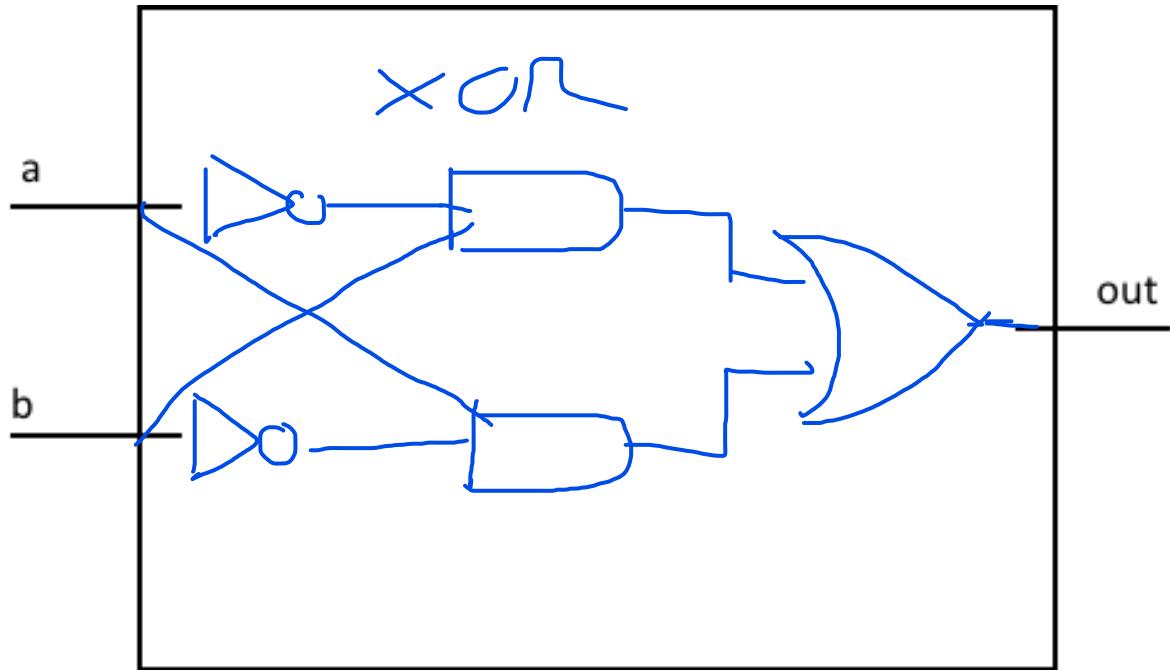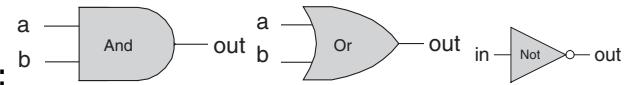Circuit Diagram**Available chips:**

[Total for Question 3: 10 marks]

Question 4

Using only And, Or and Not gates, draw the logic circuit and write HDL code for the Xnor gate. The Xnor gate for two values a and b must be implemented as: $\overline{a} \cdot \overline{b} + a \cdot b$. Clearly label the internal wires with the names used in your HDL.



HDL

```
Chip Xnor
{
    IN a, b ;
    OUT out ;
        // The available chips:
        // And(a=? ,b=? ,out=?)
        // Or(a=? ,b=? ,out=?)
        // Not(in=? ,out=?)
```

PARTS:

// write your HDL code in this box

}

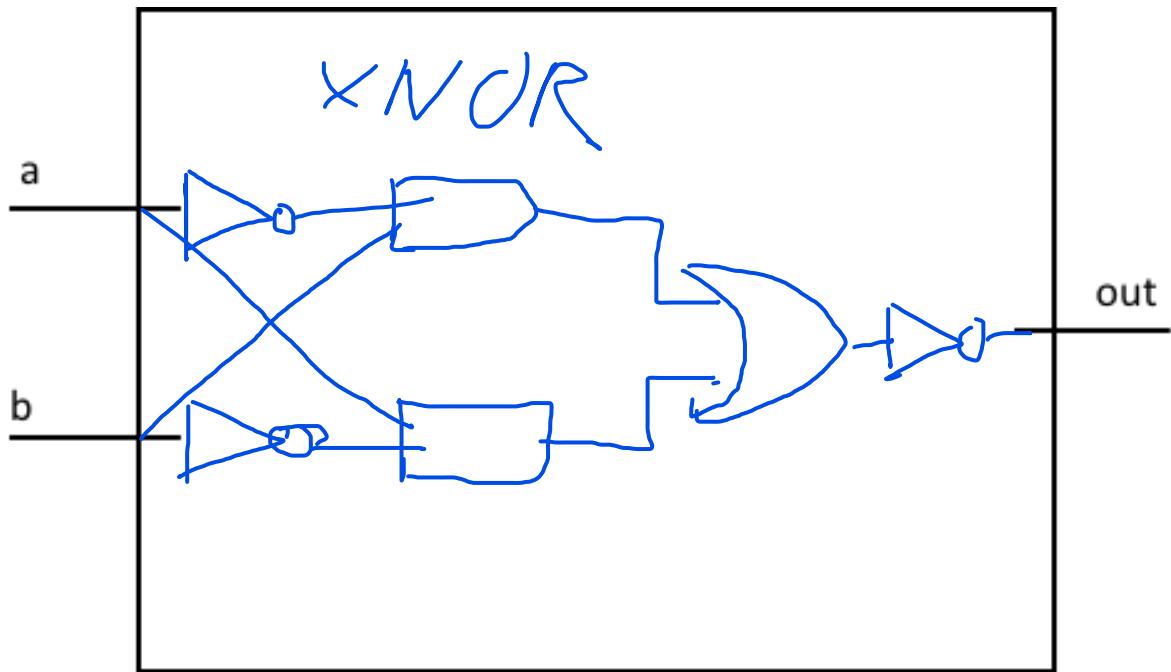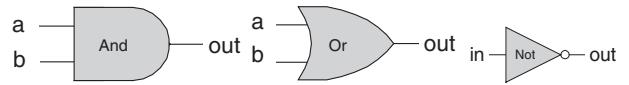Circuit Diagram**Available chips:**

[Total for Question 4: 10 marks]

Question 5

Using only And, Or and Not gates, draw the logic circuit and write HDL code for the Mux gate. The Mux gate with two inputs **a**, **b** and a selector **sel** must be implemented as: $sel \cdot b + \overline{sel} \cdot a$. Clearly label the internal wires with the names used in your HDL.



HDL


```
Chip Mux
{
    IN a, b, sel;
    OUT out;
} // The available chips:
// And(a=? ,b=? ,out=?)
// Or(a=? ,b=? ,out=?)
// Not(in=? ,out=?)
```

PARTS:

// write your HDL code in this box

}

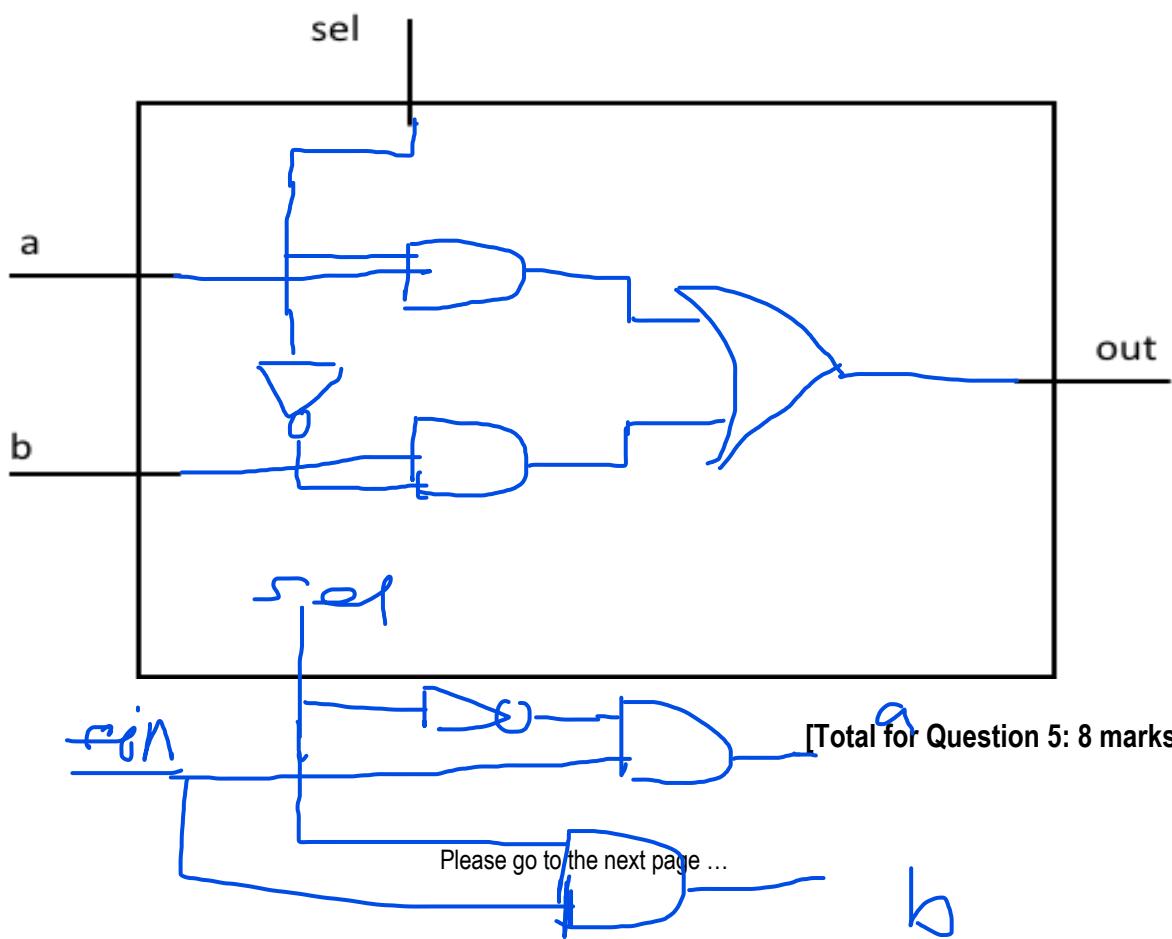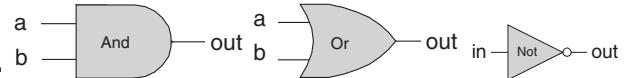Circuit Diagram**Available chips:**

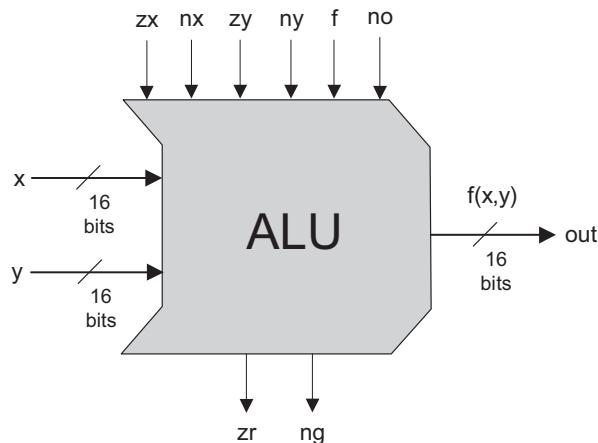Question 6

zx	nx	zy	ny	f	no
if zx==0 then x1=x else x1=0	if nx==0 then x2=x1 else x2=!x1	if zy==0 then y1=y else y1=0	if ny==0 then y2=y1 else y2=!y1	if f==0 then fout=x2&y2 else fout=x2+y2	if no==0 then out=fout else out=!fout

- a) What are the values x_1 , x_2 , y_1 , y_2 , fout and out when the ALU control inputs have the following values?

Note: Your answers must be expressed as arithmetic expressions using only the values, (**x**, **y**, **0** and **1**) and the operators (+ and -).

- if **zx** == 0 then $x_1 = \boxed{x}$, then if **nx** == 0 then $x_2 = \boxed{ }$
- if **zy** == 1 then $y_1 = \boxed{0}$ then if **ny** == 1 then $y_2 = \boxed{-1}$
- if **f** == 1 then $\text{fout} = \boxed{x - 1}$ then if **no** == 0 then $\text{out} = \boxed{x - 1}$


[6 marks]

- b) Indicate the values of the outputs **zr** and **ng** if the values of **x** and **y** are as follow?

- if **x** == 1 and **y** == 2 then **zr** =
- if **x** == 1 and **y** == 2 then **ng** =

[2 marks]

[Total for Question 6: 6 marks]

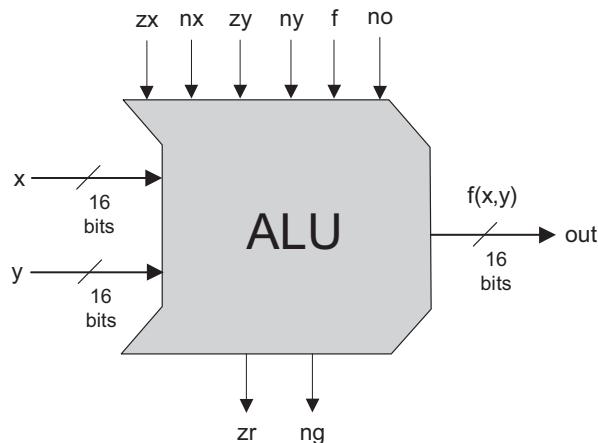Question 6

zx	nx	zy	ny	f	no
if zx==0 then x1=x else x1=0	if nx==0 then x2=x1 else x2=!x1	if zy==0 then y1=y else y1=0	if ny==0 then y2=y1 else y2=!y1	if f==0 then fout=x2&y2 else fout=x2+y2	if no==0 then out=fout else out=!fout

- c) What are the values x_1 , x_2 , y_1 , y_2 , fout and out when the ALU control inputs have the following values?

Note: Your answers must be expressed as boolean expressions using only the values, (**x**, **y**, **true** and **false**) and the operators (**&**, **|** and **!**).

- if **zx** == 0 then $x_1 = \underline{\quad} X \underline{\quad}$, then if **nx** == 0 then $x_2 = \underline{\quad} X \underline{\quad}$
- if **zy** == 1 then $y_1 = \underline{\quad} \cancel{\text{false}} \underline{\quad}$, then if **ny** == 1 then $y_2 = \underline{\quad} \cancel{\text{true}} \underline{\quad}$
- if **f** == 0 then $\text{fout} = \underline{\quad} \cancel{\text{X}} \underline{\quad}$, then if **no** == 0 then $\text{out} = \underline{\quad} \cancel{\text{X}} \underline{\quad}$

[6 marks]

- d) Indicate the values of the outputs **zr** and **ng** if the values of **x** and **y** are as follow?

- if **x** == **true** and **y** == **false** then **zr** =
- if **x** == **true** and **y** == **true** then **ng** =



false

true

[2 marks]

[Total for Question 6: 6 marks]

The following table shows the effect of 18 different combinations of control inputs to this ALU:

zx	nx	zy	ny	f	no
if zx==0 then x1=x else x1=0	if nx==0 then x2=x1 else x2=!x1	if zy==0 then y1=y else y1=0	if ny==0 then y2=y1 else y2=!y1	if f==0 then fout=x2&y2 else fout=x2+y2	if no==0 then out=fout else out=!fout
0	0	0	0	0	0
x1=x	x2=x	y1=y	y2=y	fout=x&y	out=x&y
0	0	0	0	1	0
x1=x	x2=x	y1=y	y2=y	fout=x+y	out=x+y
0	0	0	1	1	1
x1=x	x2=x	y1=y	y2=-y-1	fout=x-y-1	out=y-x
0	0	1	1	0	0
x1=x	x2=x	y1=false	y2=true	fout=x	out=x
0	0	1	1	0	1
x1=x	x2=x	y1=false	y2=true	fout=x	out=!x
0	0	1	1	1	0
x1=x	x2=x	y1=0	y2=-1	fout=x-1	out=x-1
0	0	1	1	1	1
x1=x	x2=x	y1=0	y2=-1	fout=x-1	out=-x
0	1	0	0	1	1
x1=x	x2=-x-1	y1=y	y2=y	fout=y-x-1	out=x-y
0	1	0	1	0	1
x1=x	x2=!x	y1=y	y2=!y	fout=!x&!y	out=x y
0	1	1	1	1	1
x1=x	x2=-x-1	y1=0	y2=-1	fout=-x-2	out=x+1
1	0	1	0	1	0
x1=0	x2=0	y1=0	y2=0	fout=0	out=0
1	1	0	0	0	0
x1=false	x2=true	y1=y	y2=y	fout=y	out=y
1	1	0	0	0	1
x1=false	x2=true	y1=y	y2=y	fout=y	out=!y
1	1	0	0	1	0
x1=0	x2=-1	y1=y	y2=y	fout=y-1	out=y-1
1	1	0	0	1	1
x1=0	x2=-1	y1=y	y2=y	fout=y-1	out=-y
1	1	0	1	1	1
x1=0	x2=-1	y1=y	y2=-y-1	fout=-y-2	out=y+1
1	1	1	0	1	0
x1=0	x2=-1	y1=0	y2=0	fout=-1	out=-1
1	1	1	1	1	1
x1=0	x2=-1	y1=0	y2=-1	fout=-2	out=1

Question 7

What is the largest decimal number that can be represented by a two's complement 16-bit binary number?

Answer:

z^{15-1}

$$2^{15} - 1$$

[Total for Question 7: 2 marks]

Question 8

What is the largest decimal number that can be represented by a 16-bit unsigned binary number?

Answer:

215-1217, — — — —

[Total for Question 8: 2 marks]

Question 9

What is the most negative decimal number that can be represented by a two's complement 16-bit binary number?

Answer:

-215

[Total for Question 9: 2 marks]

Question 10

What is the smallest decimal number that can be represented by an unsigned 16-bit binary number?

Answer:

5

[Total for Question 10: 2 marks]

Question 11

What is the decimal value of the 8-bit two's complement number 11101010₂?

Answer:

- 22

$$\begin{array}{r} 82 \\ \times 106 \\ \hline 59 \quad -70 \end{array}$$

[Total for Question 11: 2 marks]

Question 12

Draw the logic circuit and write the HDL implementation for a 1-bit register using Mux and DFF chips. Clearly label the chips and internal wires with the names used in your HDL.



HDL

```
Chip Bit
{
    IN in, load ;
    OUT out ;
} // The available chips:
// DFF(in=?,out=?)
// Mux(a=?,b=?,sel=?,out=?)
```

PARTS:

// write your HDL code in this box

}

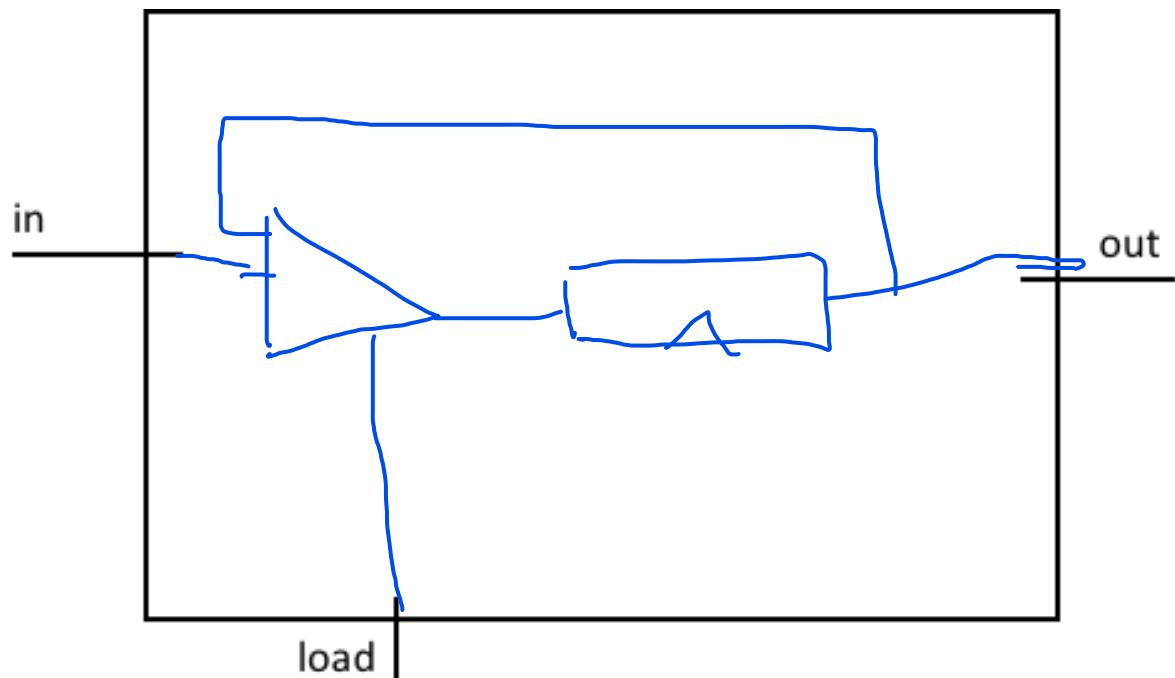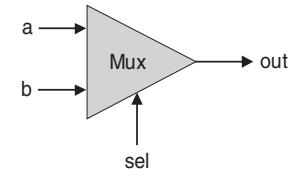Circuit Diagram**Available chips:**

[Total for Question 12: 4 marks]

Question 13

Draw the logic circuit and write the HDL implementation for a HalfAdder using Xor and And chips. Clearly label the chips and internal wires with the names used in your HDL.



HDL

```
Chip HalfAdder          // The available chips:  
{  
    IN a, b ;           // Xor(a=? ,b=? ,out=? )  
    OUT sum, carry ;   // And(a=? ,b=? ,out=? )
```

PARTS:

// write your HDL code in this box

}

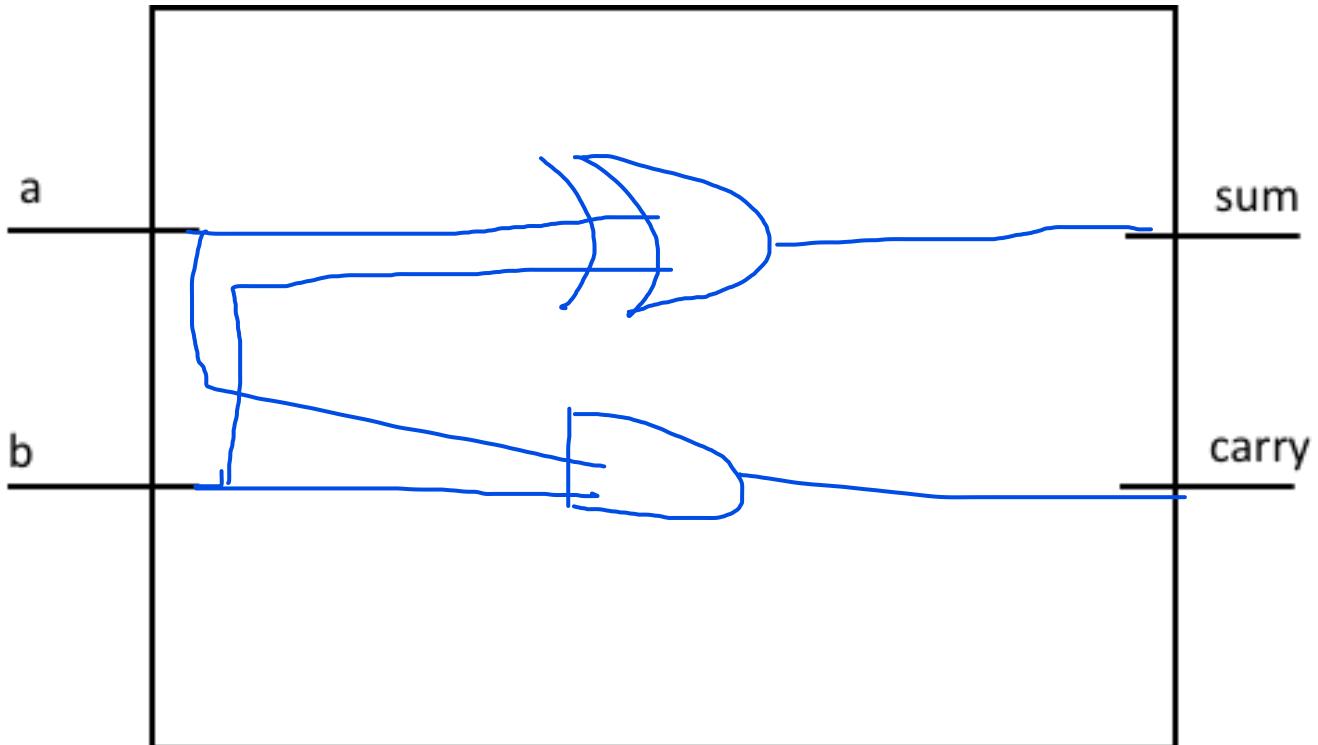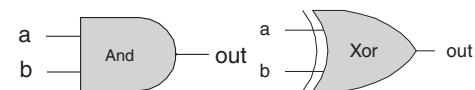Circuit Diagram**Available chips:**

[Total for Question 13: 4 marks]

Question 14

Draw the logic circuit and write the HDL implementation for a FullAdder using HalfAdder and Or chips. Clearly label the chips and internal wires with the names used in your HDL.



HDL

```
Chip FullAdder          // The available chips:  
{  
    IN a, b, c ;          // HalfAdder(a=? ,b=? ,sum=? ,carry=? )  
    OUT sum, carry ;      // Or(a=? ,b=? ,out=? )
```

PARTS:

// write your HDL code in this box

}

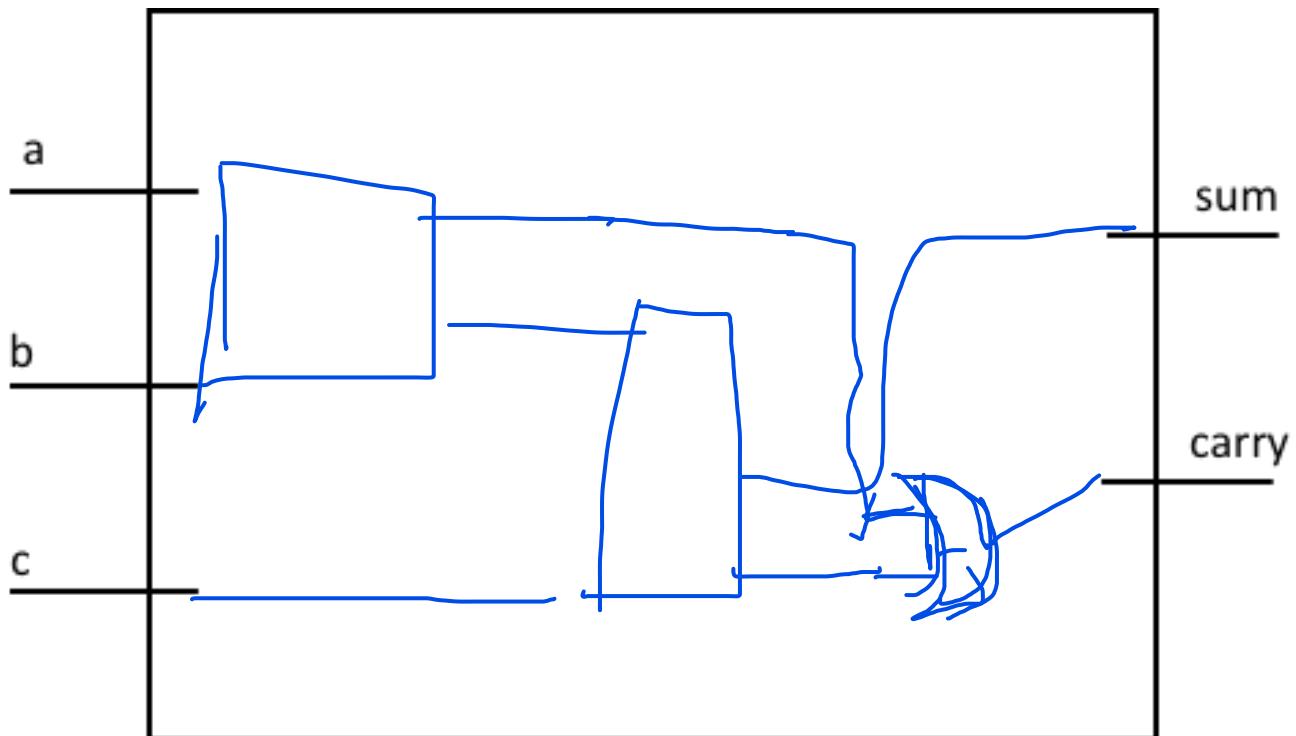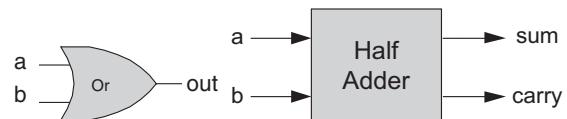Circuit Diagram**Available chips:**

[Total for Question 14: 4 marks]

Question 15

Draw the logic circuit and write HDL code for a RAM with 2 registers using Register, Mux16, and Dmux chips. Clearly label the chips and internal wires with the names used in your HDL.

HDL


```
Chip RAM
{
    IN in[16], load, address ;
    OUT out[16] ;

        // The available chips:
        // Dmux (in=? ,sel=? ,a=? ,b=?)
        // Register(in=? ,load=? ,out=?)
        // Mux16(a=? ,b=? ,sel=? ,out=?)
}
```

PARTS:

// write your HDL code in this box

}

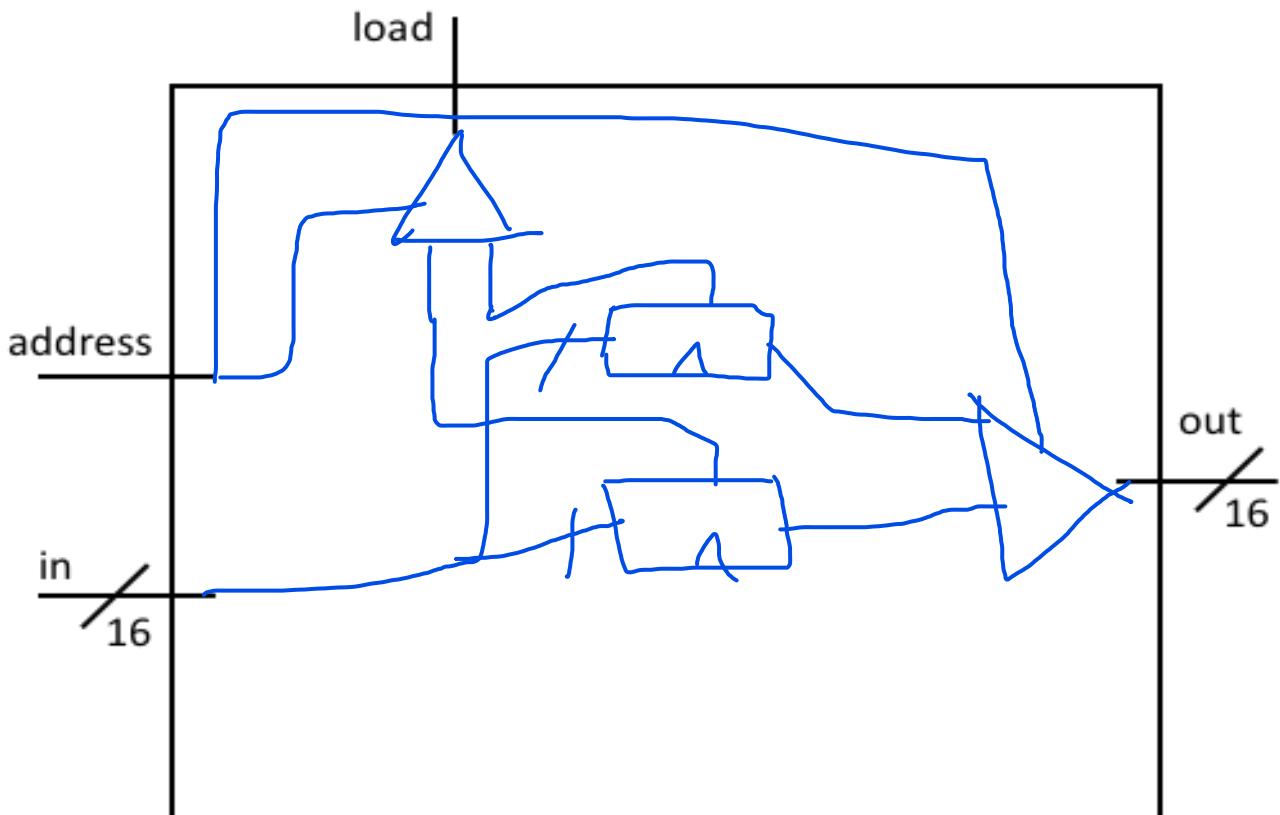Circuit Diagram

[Total for Question 15: 12 marks]

Question 16

Draw the logic circuit and write the HDL for the Hack machine's program counter, PC. Clearly label the chips and internal wires with the names used in your HDL.

HDL


```
Chip PC
{
    IN in[16], load, inc, reset;      // Register(in=?,load=?,out=?)
    OUT out[16];                   // Mux16(a=?,b=?,sel=?,out=?)
    PARTS:
        // Inc16(in=?,out=?)
}
```

// write your HDL code in this box

}

Circuit Diagram

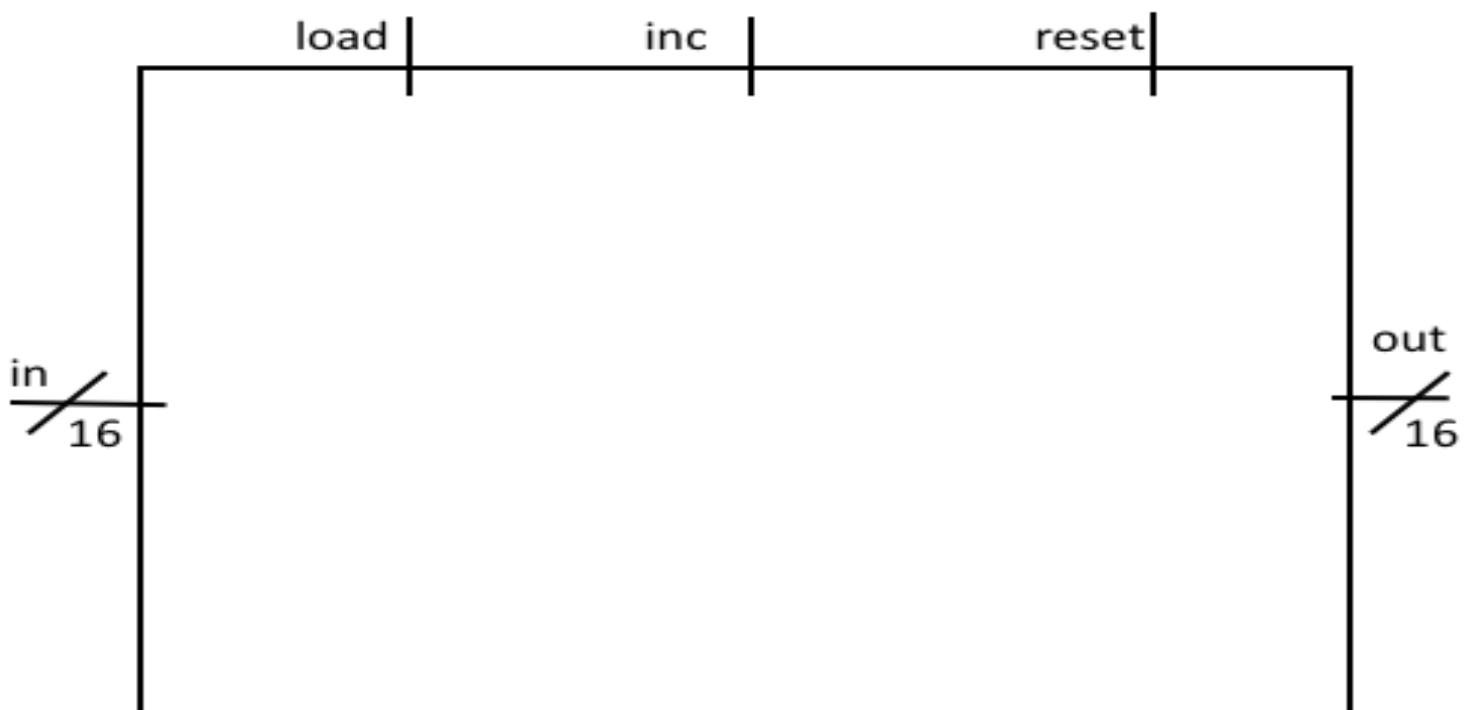Function: If $\text{reset}(t-1)$ then $\text{out}(t)=0$
 else if $\text{load}(t-1)$ then $\text{out}(t)=\text{in}(t-1)$
 else if $\text{inc}(t-1)$ then $\text{out}(t)=\text{out}(t-1)+1$
 else $\text{out}(t)=\text{out}(t-1)$



[Total for Question 16: 12 marks]

Question 17

What three kinds of symbols can appear in a Hack Assembly Language program?

1. predefined
2. label
3. var

[Total for Question 17: 6 marks]

Question 18

When are the values determined for the three kinds of symbols that can appear in Hack Assembly?

1. before 1st pass initialization
2. 1st pass
3. second pass

[Total for Question 7: 18 marks]

Question 19

Excluding predefined symbols, show the symbol table for the following Hack Assembly at the end of the first pass:

```
@R0 .
D=M .
@END .
D;JLE .
@counter
M=D .
@x .
M=D
(LOOP)
D=D+A
@LOOP
D;JGT
(END)
@END
0;JMP
```

Symbol	Value
END	13
LOOP	9

[Total for Question 19: 4 marks]

Question 20

Show the final symbol table entries for the variables in the following Hack Assembly program:

```
@R0
D=M
@END
D;JLE
@counter
M=D
@x
M=D
(LOOP)
D=D+A
@LOOP
D;JGT
(END)
@END
0;JMP
```

Symbol	Value
Counter	16
X	17

[Total for Question 20: 4 marks]

Question 21

Implement the following code fragments in Hack Virtual Machine code, the variables **a**, **b** and **c** are in the local segment at offsets 4, 5 and 6 respectively.

Jack Code

a) $a \sim (a | b)$ push to stack

Virtual Machine Code

[4 marks]

b) $(a + (b + c))$

c) $((a + b) + c)$

[5 marks]

d) Recursive.factorial(6)

D

[5 marks]

e) let a = c * b

[2 marks]

[4 marks]

[Total for Question 21: 20 marks]

Question 22

Implement the following code fragments in Hack Virtual Machine code, the variables **a**, **b** and **c** are in the local segment at offsets 4, 5 and 6 respectively.

Jack Code

a) let a = 93 ↗

b) Math.multiply(b,c) ↗ ↘

c) return 17 ↗

Virtual Machine Code

[2 marks]

[3 marks]

[2 marks]

[Total for Question 22: 7 marks]

Question 23

Complete the Hack Virtual Machine code that implements the body of the following Jack function:

Jack Code

```
function add(int x,int y)
{
    int sum ;
    let sum = x + y ;
    return sum ;
}
```

Virtual Machine Code

```
function Useful.add 1
push arg 0
push arg 1
add
pop /out 0
```

return

[Total for Question 23: 5 marks]

Question 24

Complete the Hack Virtual Machine code that implements the body of the following Jack function:

Jack Code

```
function nfib(int n)
{
    if ( n < 2 )
    {
        return 1 ;
    }

    return (1 + nfib(n-1)) + nfib(n-2) ;
}
```

Virtual Machine Code

```
function Useful.nfib 0
    push arg 0
    push const 2
    let

    not
    if-goto if_false
    push constant

    return

label if_false
    push const 1
    push local 0
    push const 1
    sub
    call Useful.nfib 1
    add
    -- 2
    add
    return
```

[Total for Question 24: 15 marks]

Question 25

Complete the Hack Virtual Machine code that implements the body of the following Jack function:

Jack Code

```
function triangle(int n)
{
    if ( n < 2 )

```

Virtual Machine Code

```
not
if-goto if_false
```

```
{
```

```
return 1;
```

```
return
```

```
}
```

```
return n + Useful.triangle(n - 1);
```

```
label if_false
```

```
}
```

```
return
```

[Total for Question 25: 10 marks]

Question 26

Write Hack Assembly Language that will implement the following Hack Virtual Machine commands:

Virtual Machine Code**Assembly Language Code**

- a) push constant 0

$\text{@ } \text{D}$
 $\text{D} = \text{A}$
 $\text{@ } \text{SP}$
 $\text{A} = \text{M}$
 $\text{M} = \text{D}$

@ SP
 $\text{AM} = \text{M}$

[5 marks]

- b) pop local 1

@ SP
 $\text{AM} = \text{M-1}$
 $\text{D} = \text{M}$

@ LCL
 $\text{A} = \text{M+1} \rightarrow \text{M} = \text{D}$

[6 marks]

- c) push argument 56

@ 56
 $\text{D} = \text{A}$
 @ SP ARG
 $\text{A} = \text{M+D}$
 $\text{D} = \text{M}$
 @ SP
 $\text{A} = \text{M}$
 $\text{M} = \text{D}$

[10 marks]

[Total for Question 26: 21 marks]

~~$\text{A} = \text{M}$~~ @ SP
 $\text{M} = \text{M+1}$

Question 27

Write Hack Assembly Language that will implement the following Hack Virtual Machine commands:

Virtual Machine Code

d) add

$\textcircled{a} \text{ SP}$
~~A = M + D = M - 1~~
 $D = M$
 $\textcircled{b} \text{ } \textcircled{c} \text{ SP}$
 $AM = M - 1$
 $M = M + D$
 $\textcircled{d} \text{ SP}$
~~AM = M + 1~~

Assembly Language Code

[5 marks]

d) sub

$\textcircled{a} \text{ SP}$
~~AM = M - 1~~
 $P = M$
 $\textcircled{b} \text{ SP}$
~~AM = M - 1~~
 $M = M - D$
 $\textcircled{c} \text{ SP}$
~~AM = M + 1~~


[5 marks]

[Total for Question 27: 10 marks]

Question 28

Draw the stack frame of the currently executing function in the Hack Virtual machine. It was passed n arguments and has k local variables, n and k are both greater than 3. Your answer must show where the ARG, LCL and SP virtual registers are pointing.

Diagram

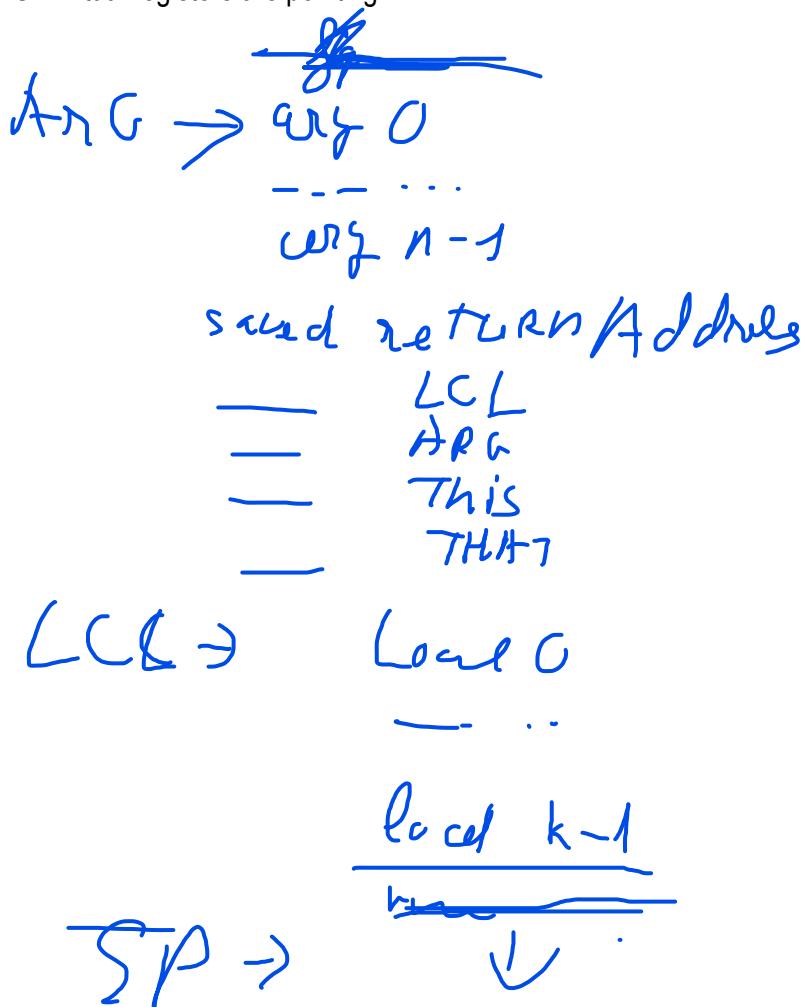

[Total for Question 28: 12 marks]